
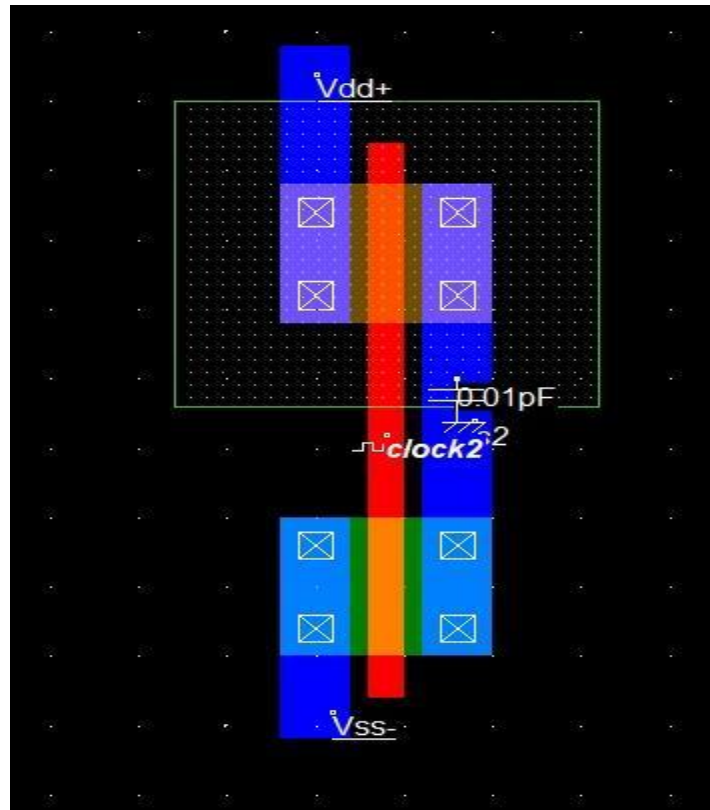



Inverter with Capacitor :

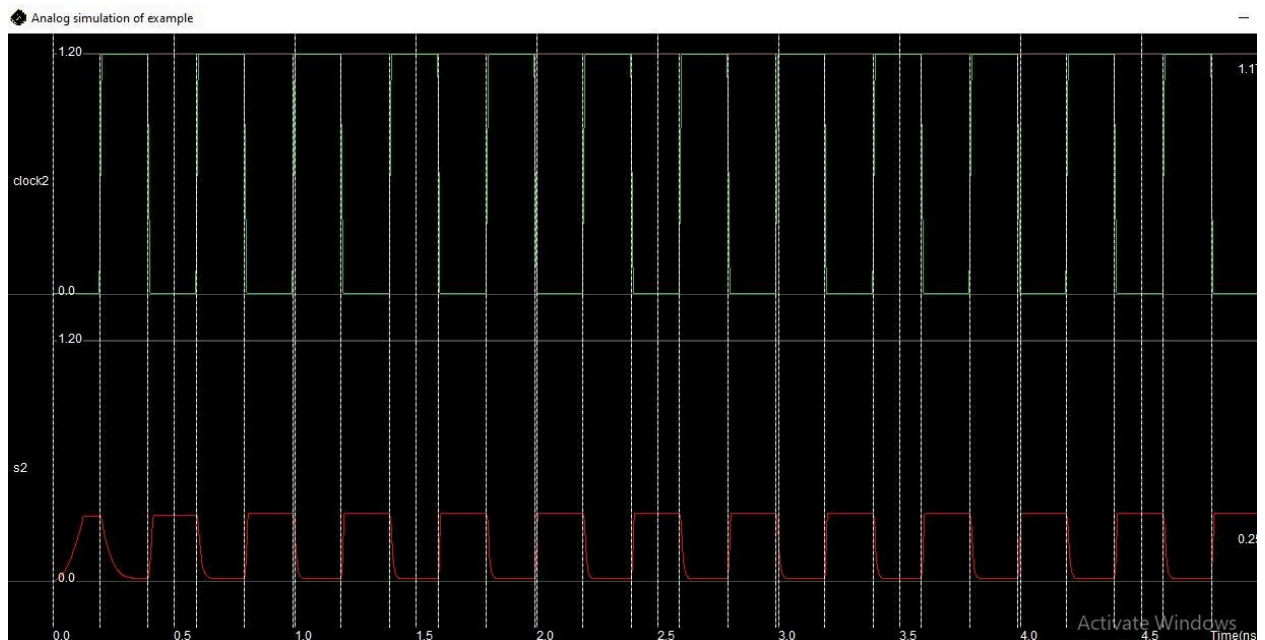


Output :




Inverter without Capacitor :

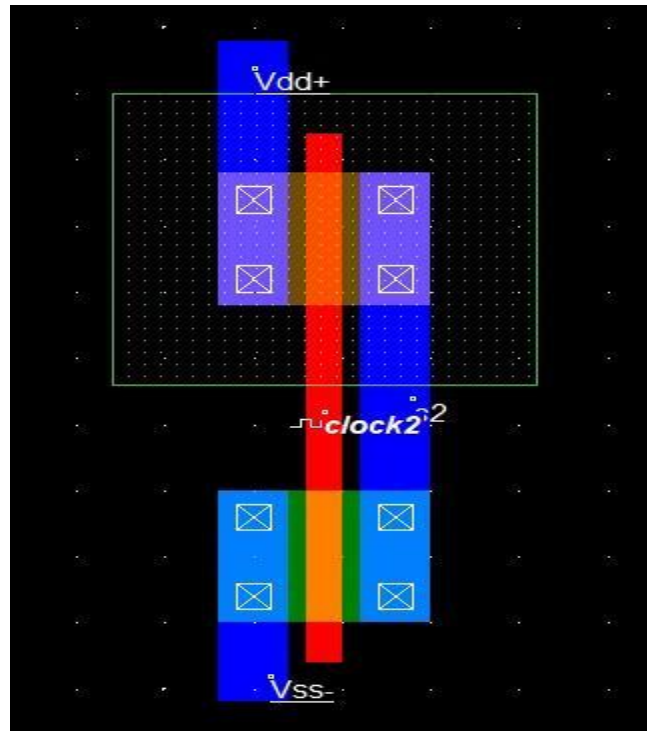


Output :

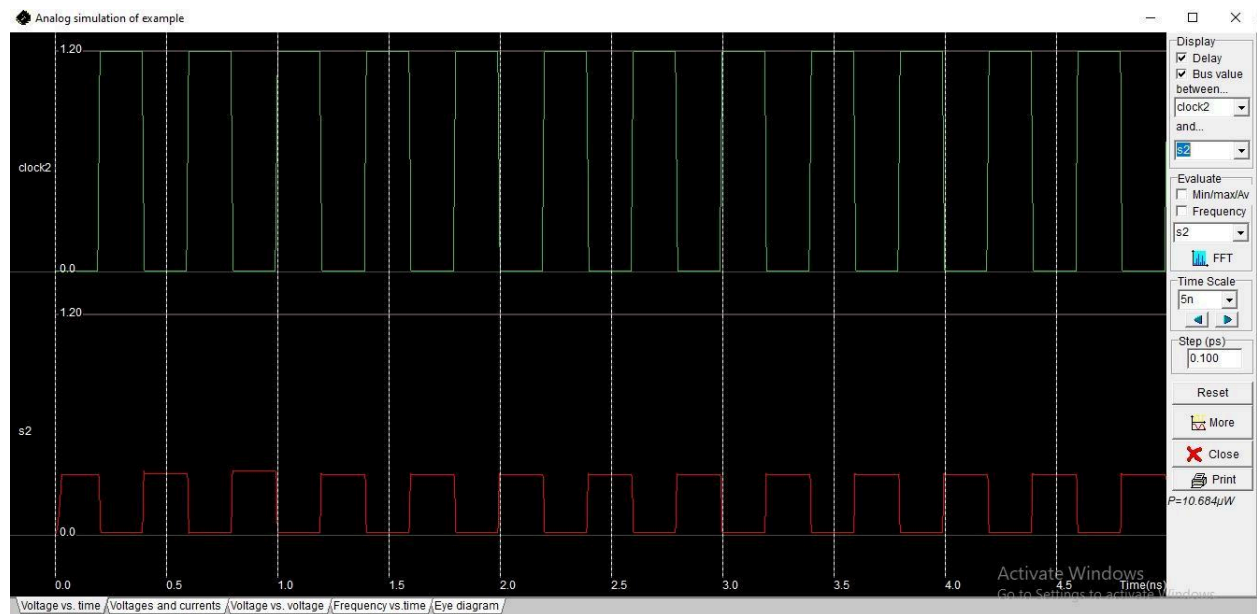


NAND with Capacitor :

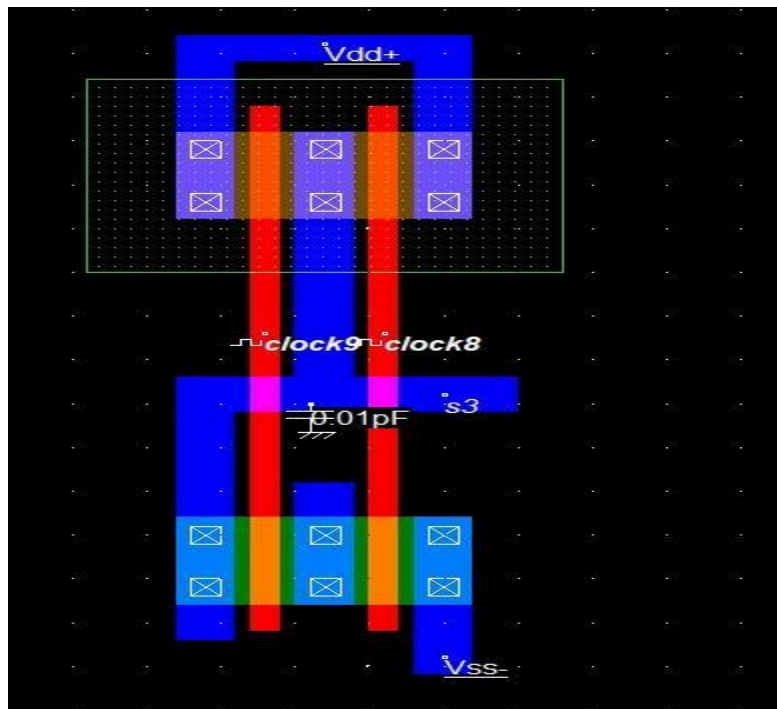


Output :

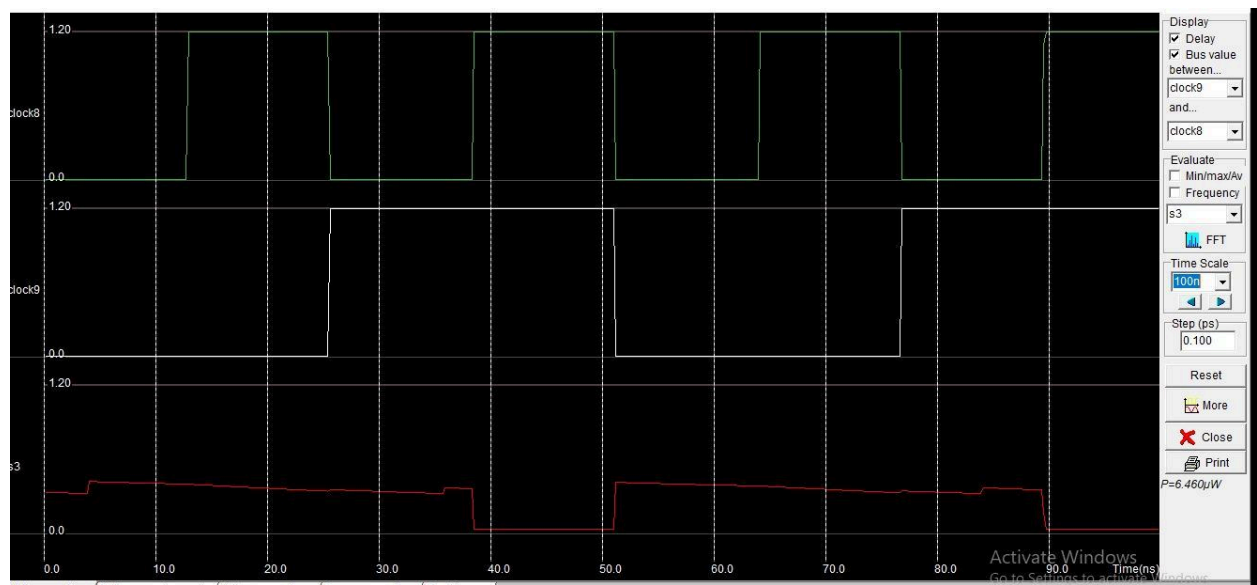


NAND without Capacitor :

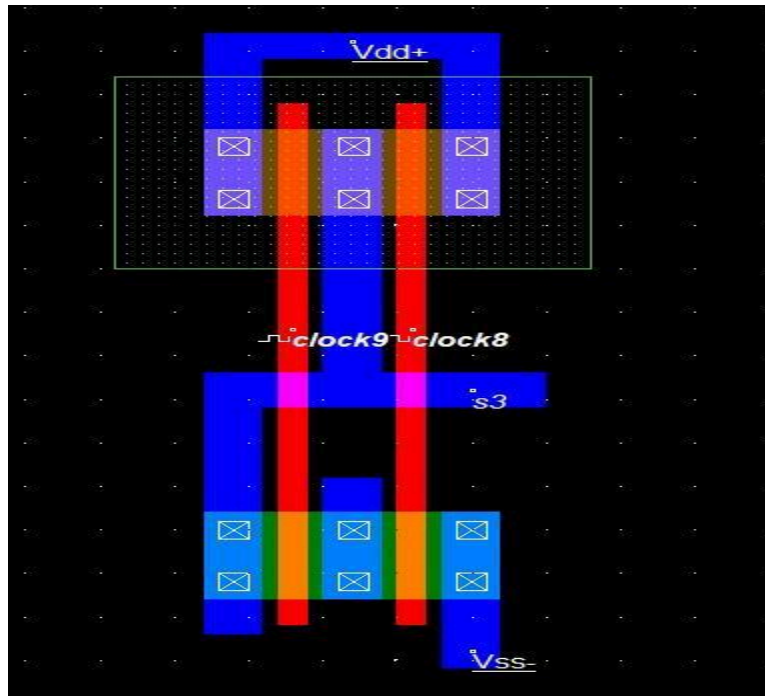

Output :

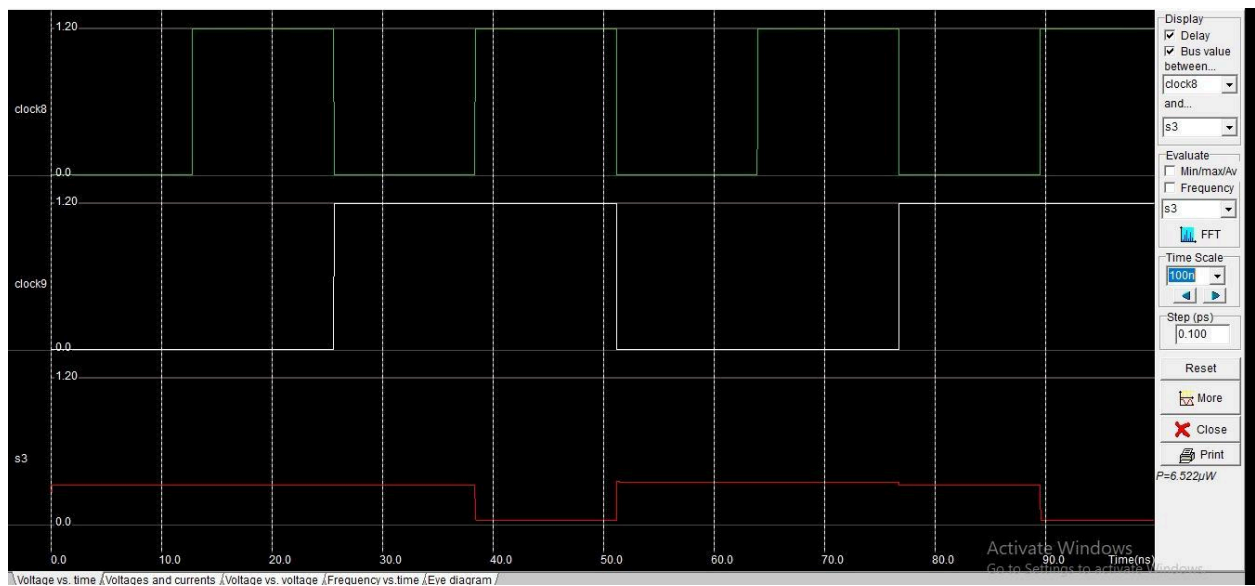


NOR with Capacitor :

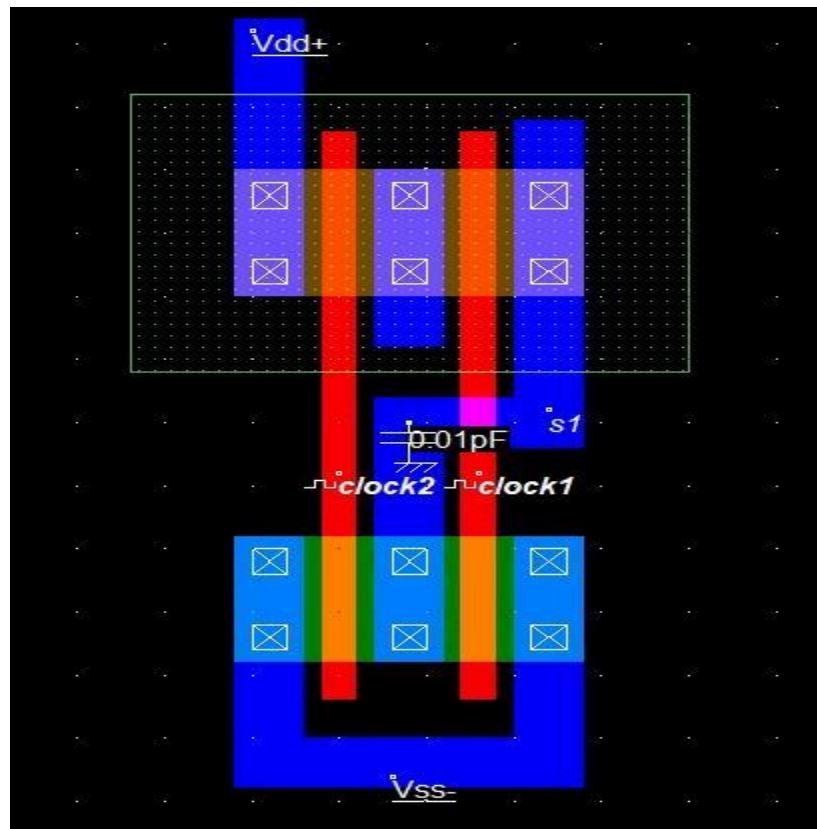

Output :



NOR without Capacitor :

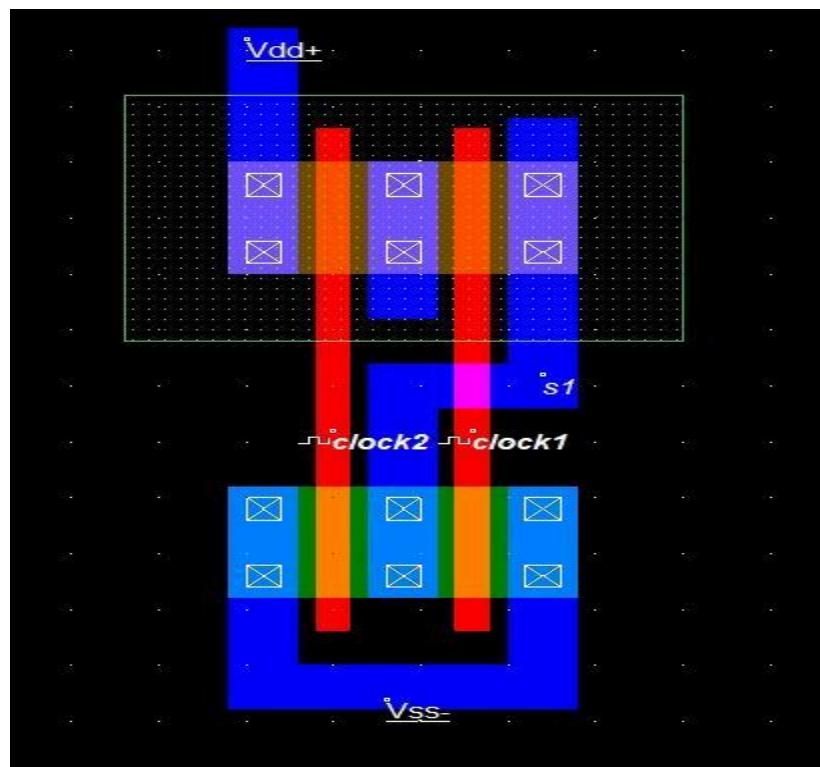

Output :

